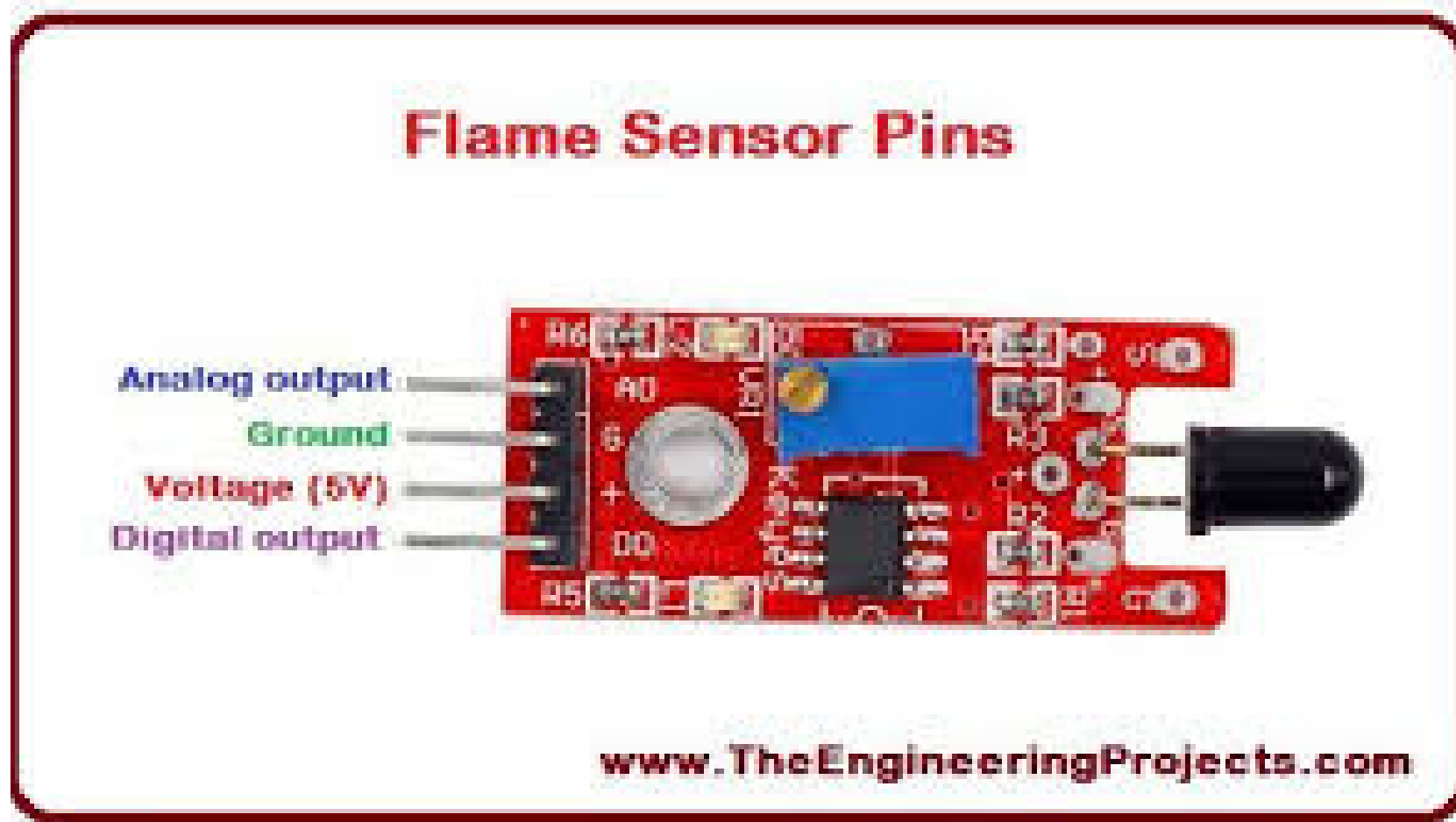




# **FIRE** **SYSTEM**

# Fire Alarm System component :

- Flame Sensor Module 4 Pins
- Buzzer Alarm 3–24V 95D



## How will we connect the system :


- 1\ connect the **gnd** of sensor to the **gnd** of esp32 in breadboard .
- 2\ connect the **voltage** of sensor to **5v** of esp in breadboard .
- 3\connect **Analog output** of sensor to ones of **analog pins** in esp32 .
- 4\ connect **Digital Output** of sensor to ones of **digital pens** .
- 5\ we need another **digital pin** for the + terminal of buzzer and - terminal for the ground .

# conclusion :


we need 3 pins of esp32 :  
analog & digital pin for **flame sensor**.  
digital pin for buzzer .

And volt of 5v .

## Simulation at Arduino uno :

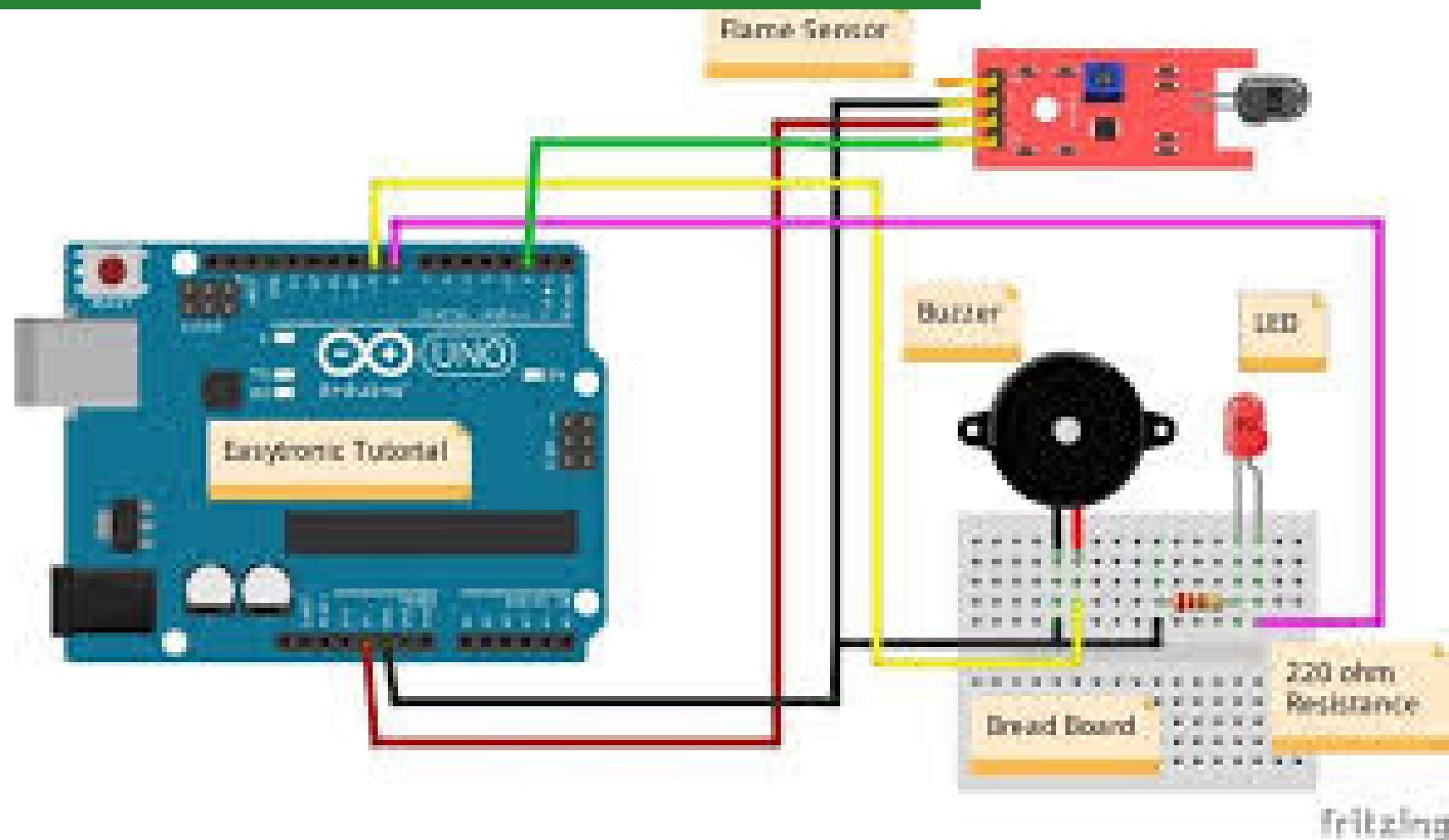

## Simulation at esp 32 :

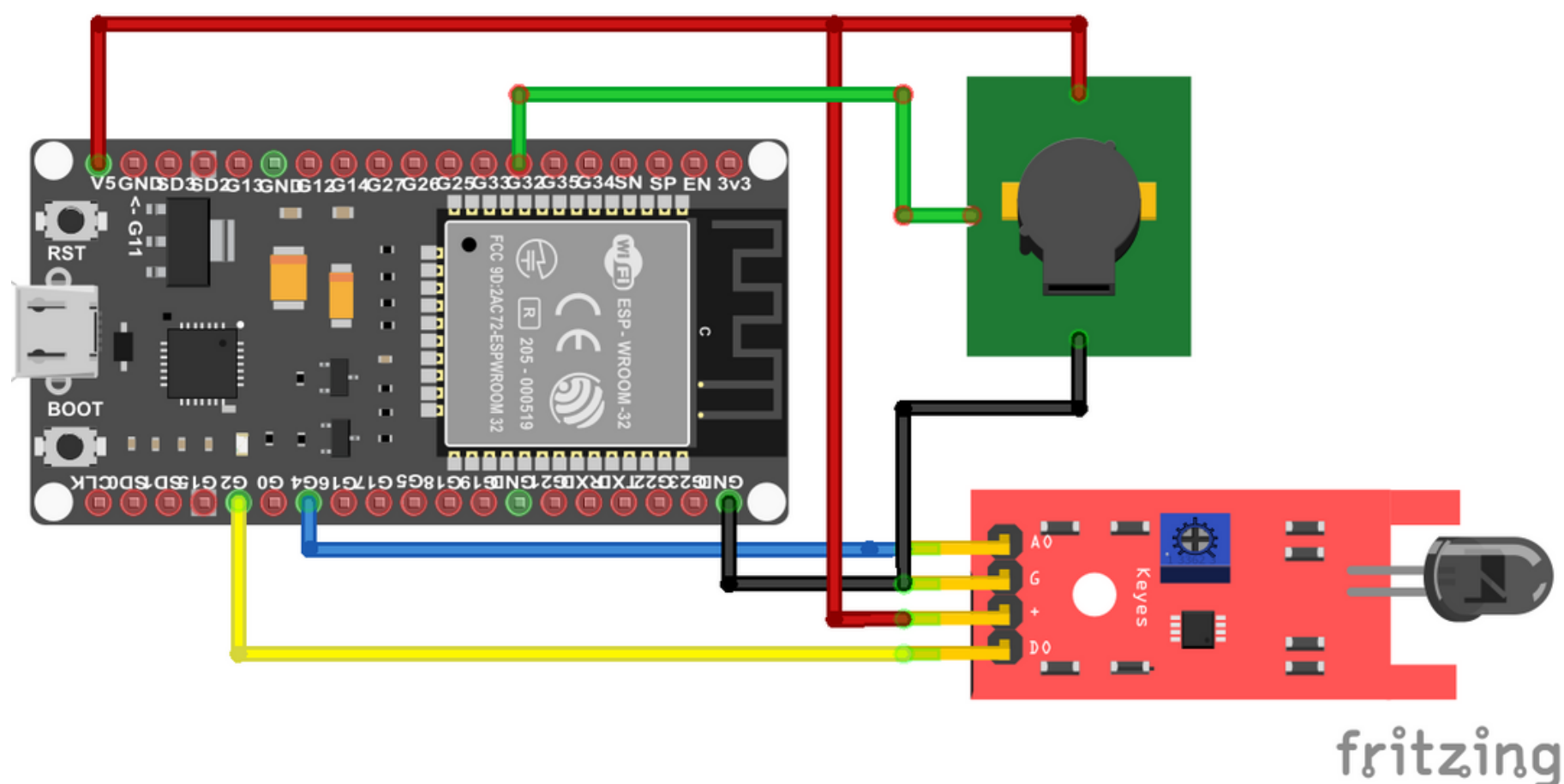

# The scenario :

1) Firstly , Our system will be in the second floor of our maquette this For ease of testing, bring the fire closer to the sensor

2)In regular conditions flame sensor is measuring a wave lenght in range of 900 to 1000 but when we bring the fire closer to the sensor wave length will dicreased to a little vales dont exceed 100.

3)This is our main idea , when wave length decreased we will make an if codition to fire the buzzer (making alarm ) and send a notification for our web server .

4)we can get benefit from the lighting system to changing the color of our led to the red color(only in condition of rgb leds ) .  
we can get benefit from the lighting system to changing the color of our led to the red color .

## Extras

5) we can regulate that when the fire occurred order the servo motor in garage and main door to open . In order not to conflict with security system, Opening the door will be only when the fire still for 5minutes or more and If the source of the fire stay away from the sensor ->close the door

6) In condition of Having servo motor in windows we can regular it with fire system as when fire occurred -> open the windows .

**THANKS..**

**ENG:AHMED HOSSAM**